

Lecture Steps: L03 Building the circuit in COMSOL

1. RC CIRCUIT THEORY

2. NODES CONCEPT

3. BUILDING THE CIRCUIT IN COMSOL