

Lecture Steps: L05 Result Analysis

1. ADD RESULT PLOT

2. PLOT CAPACITOR CURRENT

3. CHARGING OF CAPACITOR