

Lecture Steps: L18 Full wave rectifier simulation results

1. FEW CORRECTIONS

2. STUDY SETTINGS

3. PLOT RESULTS

4. PLOT INPUT AC VOLTAGE AND RECTIFIED OUTPUT