

Lecture Steps: L19 AC to DC converter

- 1. ADDING A CAPACITOR (THEORY)**
- 2. UPDATING COMSOL MODEL**
- 3. SIMULATE**
- 4. AC INPUT AND DC OUTPUT VERIFIED**