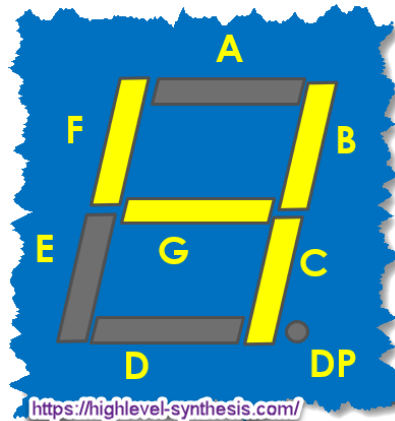


To turn on the 7-segment, the control signal connected to the PNP transistor switch should be 0.

To show the number 4, the data signal should turn on the LEDs on the four segments B, C, F and G. So, as the 7-segment configuration is common anode the data is 0b10011001



DP	G	F	E	D	C	B	A
1	0	0	1	1	0	0	1